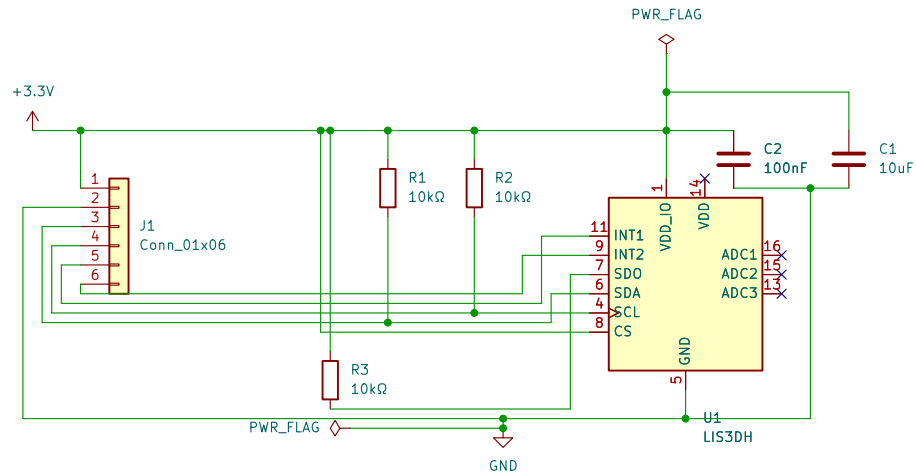




THE PURPOSE OF BOTH THE CAPACITOR IS DECOUPLING ,
TO STABILIZE THE POWER AND REMOVE ANY HIGH FREQUENCY NOISE
(10uF is a bulk decoupling , for smooth larger voltage)

R1 and R2 are I²C pull-up resistors used to,
maintain stable HIGH logic levels on the SDA and SCL lines.

SDO/SA0 is connected to GND through a pull-down resistor ,
to define a stable I²C address and avoid floating logic levels.

https://kicad.github.io/footprints/Package_LGA

<https://www.st.com/resource/en/datasheet/lis3dh.pdf>

https://www.snapeda.com/parts/LIS3DH/STMicroelectronics/view-part/?ref=search&t=LIS3DH&ab_test_case=b

Sheet: /
File: Final_Project.kicad_sch

Title:

Size: A4
KiCad E.D.A. 10.0.1

Date:

Rev:
Id: 1/1